

## EECT/CE 6325 VLSI Design

Fall 2022

### PROJECT #4: Cell Library Due: Wed. Oct. 26 (11:30 am)

#### Project Introduction

For this project you will be creating your standard library of cells (without D-Flip Flop), which will be used for your final project.

#### Project Goals

- 1) Layout and verify the following cells:
  - INV
  - NAND2
  - NOR2
  - XOR2
  - MUX2:1
  - AOI21
  - OAI22
  - AOAI211
- 2) All your cells should be placed side by side, next to each other, and have no DRC errors. All pins must be aligned horizontally with uniform spacing.
- 3) Do not use the library.lib provided for Project 2, instead generate a .lib file for the given set of cells using *PrimeLib*. For generating a library follow the instructions given in *PrimeLib by Synopsys* document uploaded on eLearning in Project 4 folder.
- 4) The height of the pMOS diffusion (RX drw layer) must accommodate 6 contacts and the height of the nMOS diffusion (RX drw layer) must accommodate 4 contacts.
- 5) Generate abstract views of your cells, use instructions given in *Abstract View Generation* document uploaded on eLearning in Project 4 folder)

#### Project Rules & Requirements

- 1) All the cells should have the same height with VDD & GND rails aligned horizontally.
- 2) The length of the channel (L) must be 70 nm
- 3) The input slew rate is 60 ps ( $0.1 \cdot V_{dd}$  to  $0.9 \cdot V_{dd}$  and vice versa)
- 4) Assume a 70 fF load capacitance when simulating.

#### What to Turn In (points are deducted for anything missing)

- 1) A cover page containing all the following information.
  - Name, NetID and project title
- 2) Each cell layout with **rulers** showing the dimensions of the cell. Part of grade depends on the clarity of your **report**.
  - Show the distance between your pins
  - Show the length of the channel
  - Show the height & width of entire cell.
- 3) Also turn in the following for each cell in your library:
  - Simulation data that shows each transistor works in each cell
- 4) Please also hand in a layout showing all your cells lined up in a row with the boundary layers touching to demonstrate that they can be placed next to each other with no problems (yes, that means run DRC).
  - Show distance between pins to verify that they have a uniform pitch.
- 5) Upload the project report on eLearning.
- 6) Upload the zipped folder containing all layouts and schematics on eLearning

#### Grading Breakdown

Correct functionality of all cells	50%
Correct pin spacing and cell sizing	20%
Report	30%